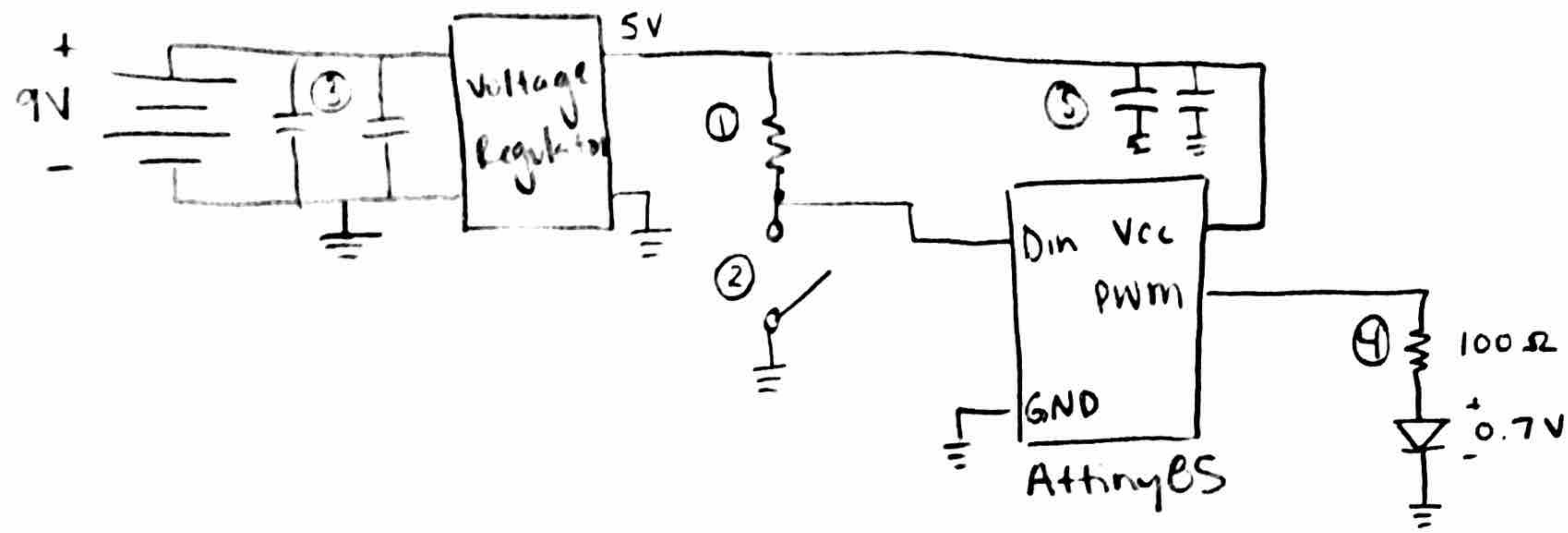


# LED Circuit

David Faulkenberry



① Pull Down Resistor

$R = 10K\Omega$

② Button input

③ Bypass Capacitors

$C = .1\mu F \parallel 10\mu F$

④ Voltage Protection for Diode